

AC Thevenin Equivalent Circuits

Christopher Hunt


Abstract

During this lab we are investigating AC Thevenin Equivalency through a simple RLC circuit. We will first perform a theoretical analysis of a circuit, then we will recreate it in the lab and test our predicted Thevenin Voltage and Impedance. Then we will recreate the Thevenin circuit and calculate the power across the load with a variable resistor and the inverse reactive component.

Equipment

- Oscilloscope
- Function Generator
- LCR Meter
- Resistance Substitution Box

Ideal Circuit Diagram

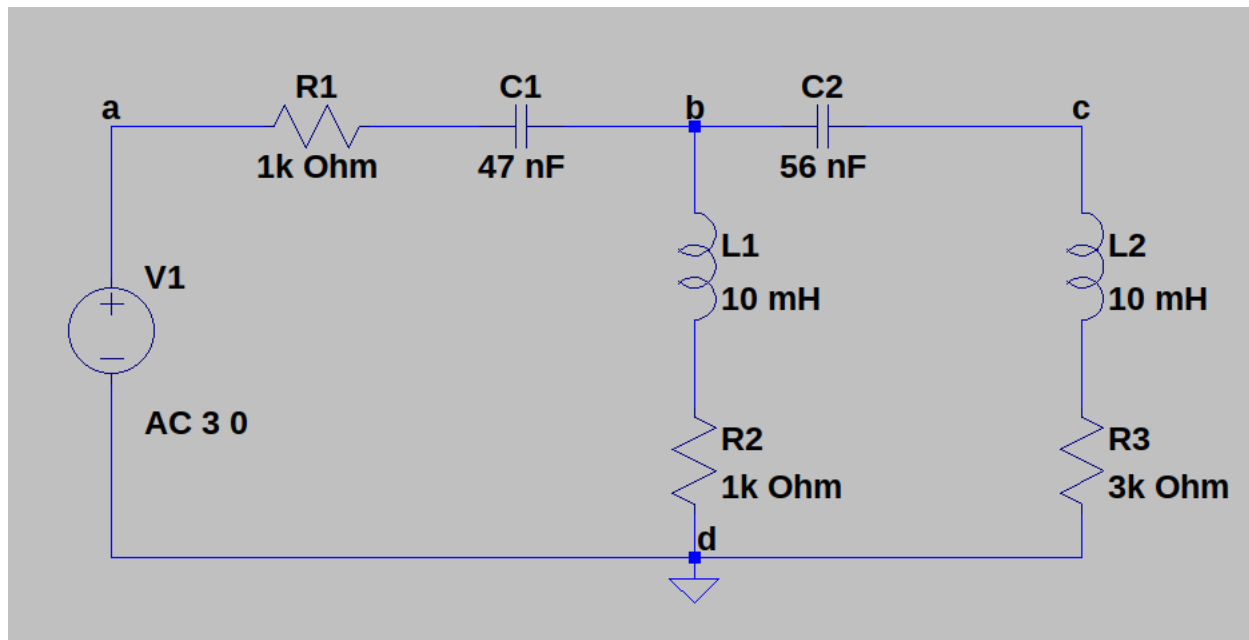

Theoretical Analysis

$R_1 = 985.6 \, \Omega$
 $R_2 = 981.2 \, \Omega$
 $C_1 = 47.68 \, \text{nF} = -j1049 \, \Omega$
 $C_2 = 58.02 \, \text{nF} = -j861.8 \, \Omega$
 $L_1 = 10.44 \, \text{mH} = j208.8 \, \Omega$

$V_s = 8 \cos(20,000t) = 8 \angle 0^\circ \text{ V}$ $\omega = 20000 \, \text{rad/s}$

Z_{Th}

$Z_{Th} = (R_1 + C_1) \parallel (R_2 + L_1) + C_2$
 $Z_{Th} = 661.3 - j998 \, \Omega$

V_{Th} $V_{Th} = V_a$ Use a voltage divider to find voltage at V_a
 $V_a = V_s \left(\frac{R_2 + L_1}{R_1 + R_2 + C_1 + L_1} \right) \Rightarrow V_a = V_{Th} = 3.07 + j2.16 = 3.75 \angle 35.14^\circ$

I_N

$I_1(-V_s + (R_1 + C_1)I_1 + (R_2 + L_1)(I_1 - I_N)) = 0$
 $(R_1 + C_1)I_1 + (R_2 + L_1)I_1 + (-R_2 - L_1)I_N = V_s$
 $(1966.8 - j840.2)I_1 + (-981.2 - j208.8)I_N = V_s$
 $(R_2 + L_1)(I_N - I_1) + C_2 I_N = 0$
 $(R_2 + L_1 + C_2)I_N + (-R_2 - L_1)I_1 = 0$
 $(981.2 - j653)I_N + (-981.2 - j208.8)I_1 = 0$

$\begin{bmatrix} 1966.8 - j840.2 & -981.2 - j208.8 \\ -981.2 - j208.8 & 981.2 - j653 \end{bmatrix} \begin{bmatrix} I_1 \\ I_N \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$
 $\begin{bmatrix} I_1 \\ I_N \end{bmatrix} = \begin{bmatrix} 2.56 \angle 2.64^\circ \\ -0.08 + j3.13 \end{bmatrix} \text{ mA}$
 $I_N = -0.08 + j3.13 = 3.13 \angle 88.5^\circ \text{ mA}$

Experimental Analysis

Component Values:

$$R_1 = 985.6\Omega \quad R_2 = 981.2\Omega \quad C_1 = 47.68nF \quad C_2 = 58.02nF \quad L_1 = 10.439mH$$

$$R_3 = 2958\Omega \quad L_2 = 10.45mH$$

AC Source:

$$V_s = 8\cos(2\pi * f * t) \text{ v} \quad f = 3184Hz$$

1

Construct the circuit shown in Figure 1 and Measure the voltage across the load. Then using that voltage, calculate the current. We will use these measurements to verify the operation of the Thevenin Equivalent to be constructed.

With the load connected to V_s , CH_1 connected to V_a and Ch_2 connected to node c. A value of 3.00 v at a phase of 51 degrees was measured.

$$V_L = 3\angle 51^\circ \text{ v}$$

Find I_L using V_L and Z_L :

$$I_L = \frac{V_L}{Z_L} \rightarrow I_L = \frac{3\angle 51^\circ}{2958 + j209.019\Omega} \rightarrow I_L = 0.691 + j0.739 \text{ mA} = 1.01\angle 46.9^\circ \text{ mA}$$

2

Disconnect the load and measure the open circuit voltage and the short circuit current. Use this to determine the Thevenin and Norton equivalent circuits.

Place Ch_2 to node b to measure open circuit voltage, V_{oc} :

$$V_{oc} = 3.74\angle 34.6^\circ$$

Then short node c to node d and place Ch_2 to node b to find I_{sc} .


$$V_b = 2.69\angle 1.2^\circ$$

$$I_{sc} = \frac{V_b}{Z_{c2}} \rightarrow I_{sc} = \frac{2.69\angle 1.2^\circ}{-j862.45} = 3.11\angle 91.2^\circ \text{ mA}$$

$$V_{Th} = V_{oc} \quad I_N = I_{sc} \quad Z_{th} = \frac{V_{Th}}{I_N} = \frac{3.74\angle 34.6^\circ \text{ v}}{3.11\angle 91.2^\circ \text{ mA}} = 1202.57\angle -56.6^\circ \Omega = 661.99 - j1003.96\Omega$$

3

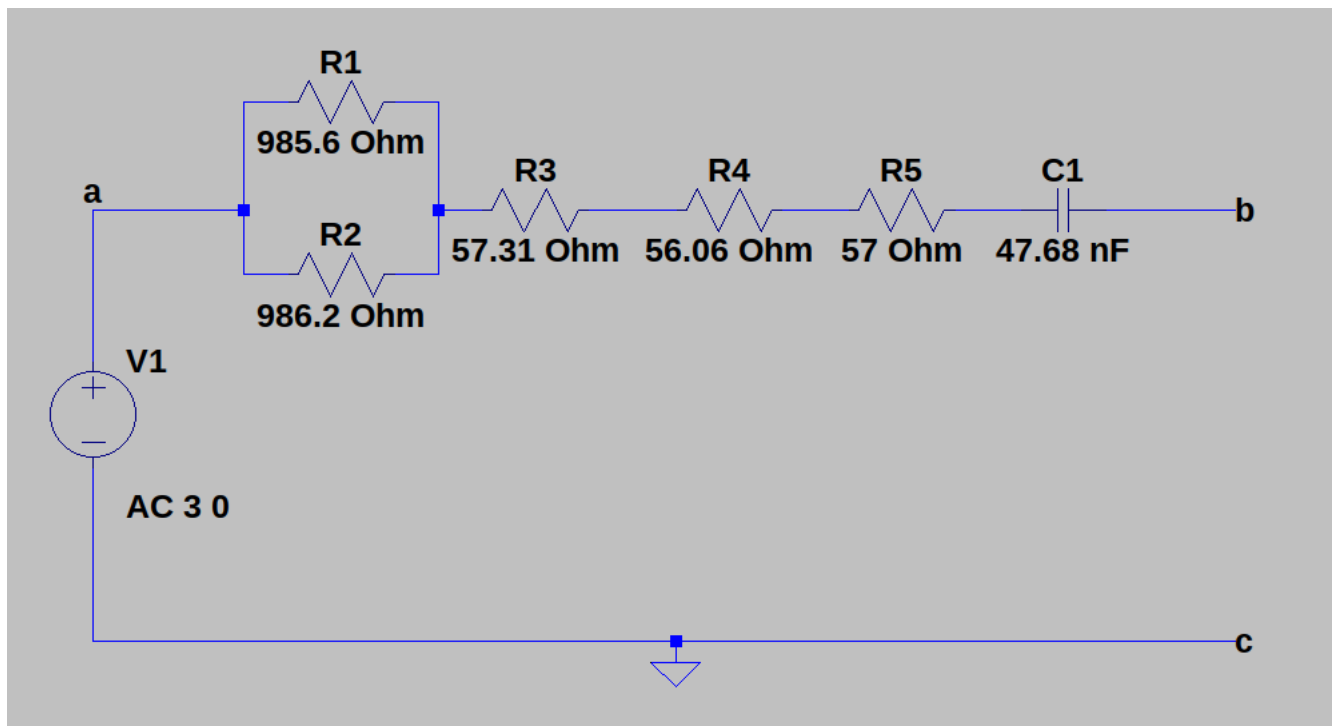Construct the Thevenin equivalent circuit.



4

Reattach the load as in the initial circuit, measure the voltage across the load, and then calculate the current.

Ch_2 at node a:

$$V_a = 2.94 \angle 16.8^\circ \text{ v} \quad Z_L = 2958 + j209.02 \, \Omega$$

$$I_L = \frac{V_a}{Z_L} = \frac{2.94 \angle 16.8}{2965.38 \angle 4.04} \rightarrow I_L = .99 \angle 12.76 \text{ mA}$$

5

Remove the load and connect the variable resistor and compensating reactance as determined from above. Vary the load resistance and calculate the voltage across the total load and just across the variable resistor.

6


Calculate the current using the voltage across the variable resistor. From this calculate power.

Data

Voltages Across Load and Variable Resistor; Calculated Current and Average Power

R_rsb (ohm)	V_L (v)	V_rsb (v)	I_L (mA)	Average Power (mW)
100	4.02 \angle 74	0.56 \angle -1	5.60 \angle -1	2.91
200	3.78 \angle 68	0.88 \angle 1	4.40 \angle 1	3.25
300	3.62 \angle 65	1.13 \angle 0	3.77 \angle 0	2.88
400	3.46 \angle 60	1.29 \angle 0	3.23 \angle 0	2.36
500	3.38 \angle 56	1.53 \angle 0	3.06 \angle 0	2.89
600	3.30 \angle 52	1.65 \angle 0	2.75 \angle 0	2.79
700	3.22 \angle 49	1.77 \angle 0	2.53 \angle 0	2.67
800	3.22 \angle 47	1.93 \angle 0	2.41 \angle 0	2.65
900	3.18 \angle 44	2.01 \angle 0	2.23 \angle 0	2.55
1000	3.18 \angle 40	2.13 \angle 0	2.13 \angle 0	2.59
1200	3.14 \angle 37	2.25 \angle 0	1.88 \angle 0	2.36
1400	2.98 \angle 34	2.41 \angle 1	1.72 \angle 0	2.12
1600	2.99 \angle 30	2.35 \angle 1	1.47 \angle 0	1.90
1800	3.01 \angle 28	2.45 \angle 1	1.36 \angle 0	1.81
2000	3.02 \angle 26	2.53 \angle 1	1.27 \angle 0	1.72

Average Power vs. R_rsb

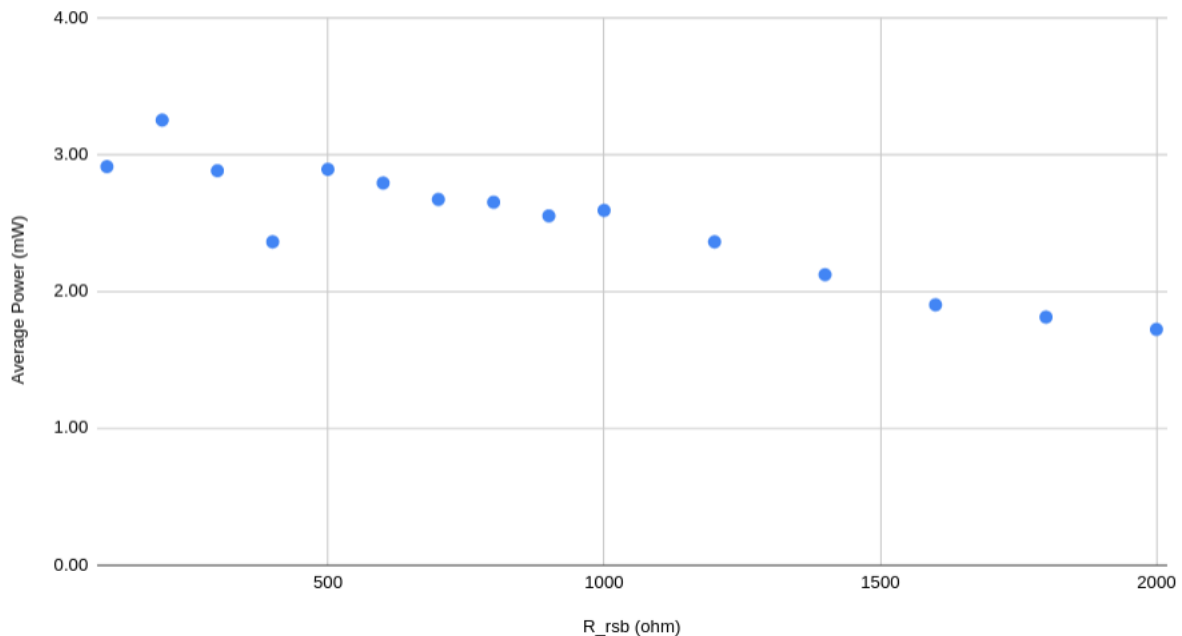

Conclusion

When comparing the values of the Thevenin equivalent circuit calculated theoretically to the experimentally measured values we measured a near match. When recreating the calculated Thevenin

equivalent with the same load the voltage and current across the load closely matched the theoretical work. During the second part of the lab, when calculating the power across a load with the appropriate compensating reactance to the Thevenin impedance, there was some curious anomalies. When the resistance was set between 100-300 ohms there was a higher than expected average power that was calculated. From the theoretical model for AC circuit max power, when the load's impedance has equal compensating reactance to the power source circuit, the power absorbed by the load reaches its max power when the load resistance matches the Thevenin resistance. In the calculations taken during this lab this pattern is not corroborated. The max power transferred is when the variable resistor was at 200 ohms, so a total load impedance of $365.4 + j1062.76 \Omega$. There is a peak at the 500 ohms load resistance, though, when we would expect to see max power transfer. Power then tapers lower and lower as the resistance increases, as expected. Although some of the data corroborated the validity of the max power transfer model, more testing would need to be done to fully verify and rule out errors made while collecting data from the test circuit.